



# NORTH SOUTH UNIVERSITY

CSE-231 Digital Logic Design

Section: 07

Faculty: MD. SHAHRIAR HUSSAIN (HSM)

## Project Fall 2021

Name: Ferdous Hasan Zihad Akash

ID: 2021309642

Date of Submission: 1st<sup>th</sup> January, 2022

Contents:

### Part 1: Combinational part

- Basic gates implementations
- Universal gate(NAND) implementation(page
- Decoder implementation
- Multiplexer implementation(page-

### Part 2: Sequential part:

- Decoder Sequential circuit implementation

---


*For Instructor's use only*

SCORE:	REMARKS:
PENALTY:	

Name:- Feridous Hasan Zihad Akash

ID:- 2021309642

Project:-

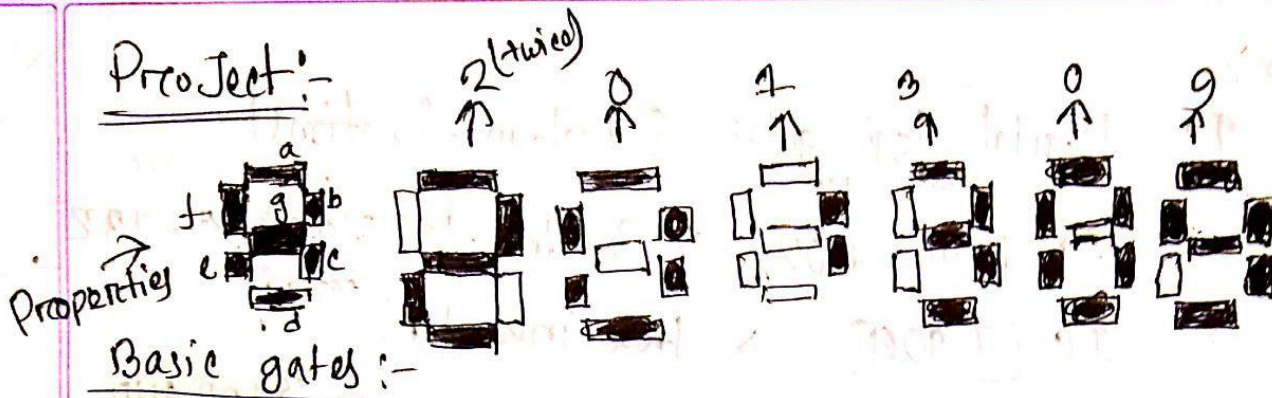

ID	A	B	C	a	b	c	d	e	f	g
2	0	0	0	1	1	0	1	1	0	1
0	0	0	1	1	1	1	1	1	1	0
2	0	1	0	1	1	0	1	1		1
1	0	1	1	0	1	1	0	0	0	0
3	1	0	0	1	1	1	1	0	0	1
0	1	0	1	1	1	1	1	1	1	0
9	1	1	0	1	1	1	1	0	1	1
	1	1	1	x	x	x	x	x	x	x

equation for:-

$$a = \sum(1110111x)$$

$$b = \sum(1111111x)$$

$$c = \sum(0101111x)$$

$$d = \sum(1110111x)$$

$$e = \sum(1110010x)$$

$$f = \sum(0100011x)$$

$$g = \sum(1010101x)$$



Solving K-map:- (basic gate)

$$a = \sum (1, 1, 1, 0, 1, 1, 1, X)$$

	$\bar{B}$		$B$	
$\bar{A}$	1	1	0	1
$A$	1	1	X	1

$$a = \bar{B} + \bar{C}$$

$$b = \sum (1, 1, 1, 1, 1, 1, 1, X)$$

	$\bar{B}$		$B$	
$\bar{A}$	1	1	1	1
$A$	1	1	X	1

$$b = 1$$

$$c = \sum (0, 1, 0, 1, 1, 1, 1, X)$$

	$\bar{B}$		$B$	
$\bar{A}$	0	1	1	0
$A$	1	1	X	1

$$c = \bar{C} + A$$

$$d = \sum (1, 1, 1, 0, 1, 1, 1, X)$$

	$\bar{B}$		$B$	
$\bar{A}$	1	1	0	1
$A$	1	1	X	1

$$d = \bar{B} + \bar{C}$$

$$e = \sum (1, 1, 1, 0, 0, 1, 0, X)$$

	$\bar{B}$		$B$	
$\bar{A}$	1	1	0	1
$A$	0	1	X	0

$$e = \bar{A}\bar{C} + \bar{B}C$$

$$f = \sum (0, 1, 0, 0, 0, 1, 1, X)$$

	$\bar{B}$		$B$	
$\bar{A}$	0	1	0	0
$A$	0	1	X	1

$$f = \bar{B}C + AB$$

$$g = \sum (1, 0, 1, 0, 1, 0, 1, X)$$

	$\bar{B}$		$B$	
$\bar{A}$	1	0	0	1
$A$	1	0	0	1

$$g = \bar{C}$$

equation for Basic gates:-

$$a = B + C$$

$$b = 1$$

$$c = C + A$$

$$d = \overline{B} + \overline{C}$$

$$e = \overline{A}\overline{C} + \overline{B}C$$

$$f = \overline{B}C + AB$$


$$g = \overline{C}$$

## Universal gate implementation:-


For universal gate I've used the basic equation then I converted those equations to NAND gate which is a universal gate.

For AND

→ used:-

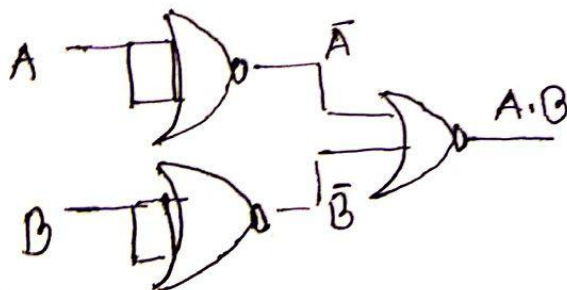

For OR

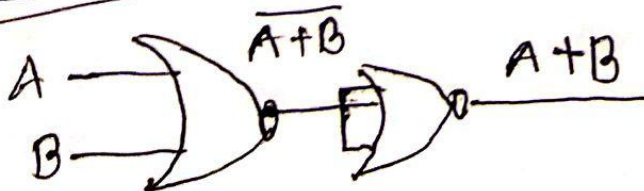

Using Decoder:-

used minterms from the basic gate:-  
Simplified equations.

eq:-

$$a = \sum (1110111x)$$

$$b = \sum (1111111x)$$

$$c = \sum (0101111x)$$

$$d = \sum (1110111x)$$

$$e = \sum (1110010x)$$

$$f = \sum (0100011x)$$



$$g = \sum (1010101x)$$



Using Max:-

$$\Sigma(1110111X)$$

$$a =$$

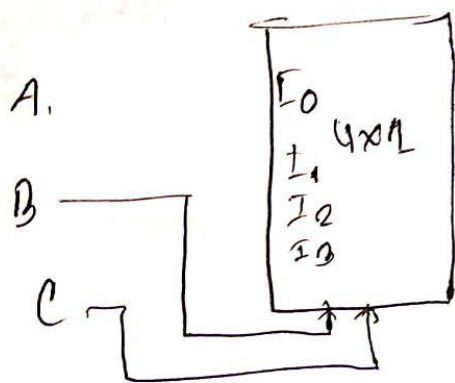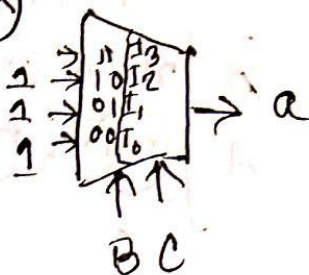

$$b = \Sigma(1111111X)$$

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{A}$	$m_0$	$m_1$	$m_2$	$m_3$
$A$	$m_4$	$m_5$	$m_6$	$m_7$
	1	1	1	$\bar{A}$

$$d = \Sigma(1110111X)$$

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{A}$	$m_0$	$m_1$	$m_2$	$m_3$
$A$	$m_4$	$m_5$	$m_6$	$m_7$
	1	1	1	0

$ABC$	
000	
001	
010	
011	
100	
101	
110	
111	

$a =$

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{A}$	$m_0$	$m_1$	$m_2$	$m_3$
$A$	$m_4$	$m_5$	$m_6$	$m_7$
	1	1	1	0

$$c = \Sigma(0101111X)$$

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{A}$	$m_0$	$m_1$	$m_2$	$m_3$
$A$	$m_4$	$m_5$	$m_6$	$m_7$
	$A$	1	$A$	$\bar{A}$

$$e = \Sigma(1110010X)$$

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{A}$	$m_0$	$m_1$	$m_2$	$m_3$
$A$	$m_4$	$m_5$	$m_6$	$m_7$
	$\bar{A}$	1	$\bar{A}$	0

$$f = \sum (0100011x)$$

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{A}$	$m_0$	$\textcircled{m_1}$	$m_2$	$m_3$
$A$	$m_4$	$\textcircled{m_5}$	$\textcircled{m_6}$	$m_7$
	0	1	A	0

$$g = \sum (1010101x)$$

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{A}$	$\textcircled{m_0}$	$m_1$	$\textcircled{m_2}$	$m_3$
$A$	$\textcircled{m_4}$	$m_5$	$\textcircled{m_6}$	$m_7$
	1	0	1	0



equation for MUX:-

$$a = 1110$$

$$b = 111\bar{A}$$

$$c = A1A\bar{A}$$

$$d = 1110$$

$$e = \bar{A}1\bar{A}0$$

$$f = 01A0$$

$$g = 1010$$

Synchronous counter:-

State Diagram:-

2 → 0 → 2 → 1 → 3 → 0 → 9 → 0

State table:-

$A(t) B(t) C(t)$	$A(t+1) B(t+1) C(t+1)$	$J_A K_A$	$J_B K_B$	$J_C K_C$
0 0 0	0 0 1	0X	0X	1X
0 0 1	0 1 0	0X	1X	X1
0 1 0	0 1 1	0X	X0	1X
0 1 1	1 0 0	1X	X1	X1
1 0 0	1 0 1	X0	0X	1X
1 0 1	1 1 0	X0	1X	X1
1 1 0	0 0 0	X1	X1	0X
1 1 1	X X X	X X	X X	X X

State equations:-

$$J_A = \Sigma(0001XXXX)$$

$$J_B = \Sigma(01XX01XX)$$

$$J_C = \Sigma(1X1X1X0X)$$



$$K_A = \Sigma(XXXX001X)$$

$$K_B =$$

$$K_C = \Sigma(X1X1X1XX)$$

$$\Sigma(XX01XX1X)$$

State Diagram:-

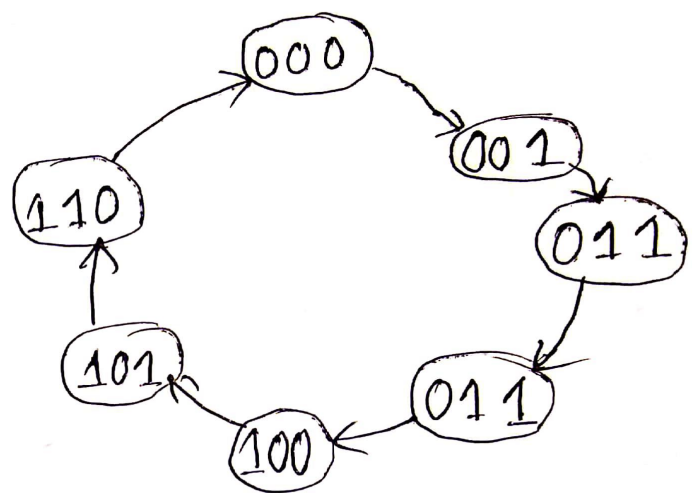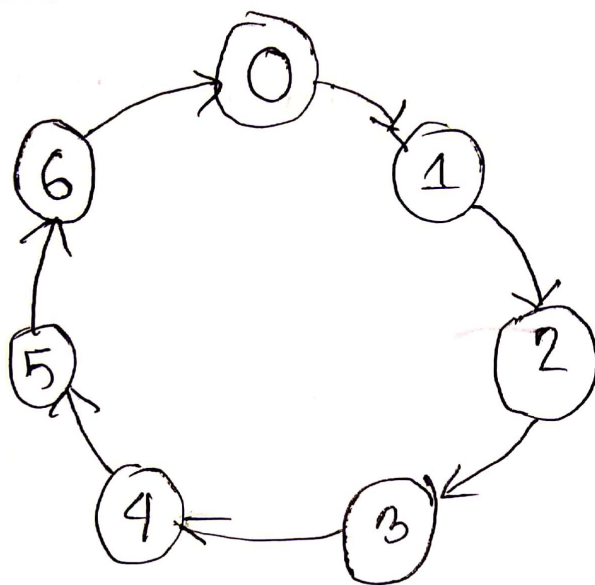



K-map for Sequential Part:-

$$J_A = \Sigma (0001xxxx)$$

A(↑)	B(↑)C(↑)		
	0	0	1
	x	x	x

$$J_A = BC$$

$$J_C = \Sigma (1x1x1x1x)$$

$$J_C = 1 \quad \bar{A} + \bar{B}$$

$$J_B = \Sigma (01xx01xx)$$

A(↑)	B(↑)C(↑)		
	0	1	x
	0	1	x

$$J_B = C$$

1	x	x	1
1	x	x	0

K-map :-

$$K_A = \sum (x \ x \ x \ x \ 0 \ 0 \ 1 \ x)$$

$$=$$

x	x	x	x
0	0	x	1

$$K_A = B_{(4)}$$

$$K_C = \sum (x \ 1 \ x \ 1 \ x \ 1 \ x \ x)$$

x	1	1	x
x	1	x	x

$$K_C = 1$$

$$K_B = \sum (x \ x \ 0 \ 1 \ x \ x \ 1 \ x)$$

x	x	1	0
x	x	x	1

$$K_B = C_{(4)} + A_{(4)}$$

equation for sequential ckt:-

$$J_A = B(t) C(t)$$

$$J_B = C(t)$$

$$J_C = \bar{A}(t) + \bar{B}(t)$$

$$K_A = B(t)$$

$$K_B = C(t) + A(t)$$

$$K_C = 1$$